

## 开关稳压器 IC 系列

## 功率损耗的计算方法（同步整流型）

此应用手册用来说明半导体器件，计算温度时使用的功率损耗。产品的温度管理关系到是否可以确保可靠性，故非常重要。

Figure 1 为同步整流 DC/DC 转换器的回路图。Figure 2 为开关节点的电压波形与电感电流波形中，损耗发生的位置。

IC 的功率损耗主要有如下 5 个因素。

1. MOSFET 的 ON 电阻造成的导通损耗  $P_{ON-L}, P_{ON-H}$
2. MOSFET 的开关损耗  $P_{SW-H}$
3. Deadtime 损耗  $P_D$
4. MOSFET 的 Gate 电荷损耗  $P_G$
5. IC 控制回路的工作损耗  $P_{IC}$

## 导通损耗

导通损耗为 Figure 2 波形中 A 区间与 B 区间的部分。A 区间时高边 MOSFET ON，低边 MOSFET OFF，损耗可由输出电流、ON 电阻及 ON 占空比算出。B 区间，高边 MOSFET OFF，低边 MOSFET ON，损耗可有输出电流、ON 电阻及 OFF 占空比算出。

导通损耗  $P_{ON-H}$  与  $P_{ON-L}$  由下式可算出。

高边 MOSFET

$$P_{ON-H} = I_O^2 \times R_{ON-H} \times \frac{V_O}{V_{IN}} \quad [W] \quad (1)$$

低边 MOSFET

$$P_{ON-L} = I_O^2 \times R_{ON-L} \times \left(1 - \frac{V_O}{V_{IN}}\right) \quad [W] \quad (2)$$

$I_O$ : 输出电流 [A]

$R_{ON-H}$ : 高边 MOSFET ON 电阻 [ $\Omega$ ]

$R_{ON-L}$ : 低边 MOSFET ON 电阻 [ $\Omega$ ]

$V_{IN}$ : 输入电压 [V]

$V_O$ : 输出电压 [V]

## 开关损耗

开关损耗为 Figure 2 波形中 C 区间与 D 区间的计算。高边、低边 MOSFET 交替 ON/OFF 时，切换 ON 的过程中，产生损耗。由于计算 2 个三角形面积与波形上升、下降过程中功率损耗求法近似，所以该计算可以近似为单纯的图形面积计算。

开关损耗  $P_{SW-H}$  如下式求得。

高边 MOSFET

$$P_{SW-H} = \frac{1}{2} \times V_{IN} \times I_O \times (t_r + t_f) \times f_{SW} \quad [W] \quad (3)$$

$V_{IN}$ : 输入电压 [V]

$I_O$ : 输出电流 [A]

$t_r$ : 高边 MOSFET 开通上升时间 [sec]

$t_f$ : 高边 MOSFET 关断下降时间 [sec]

$f_{SW}$ : 开关频率 [Hz]

低边 MOSFET，在体二极管通电期间开通，下一个 Gate 信号来时关断，负载电流沿着体二极管相同方向续流，Drain 电压保持在低电压。所以开关损耗极少。

## DeadTime 损耗

高边与低边 MOSFET 同时 ON 的话，VIN-GND 间形成短路，发生非常大的电流尖峰，所以，设置两 MOSFET 均为 OFF 的死区时间来防止短路。电感电流继续流动，死区内电感电流流经低边 MOSFET 的体二极管。Deadtime 损耗  $P_D$  可用 Figure 2 波形中 E 区间与 F 区间来计算，由下式可算出。

$$P_D = V_D \times I_O \times (t_{Dr} + t_{Df}) \times f_{SW} \quad [W] \quad (4)$$

$V_D$ : 低边 MOSFET 的

体二极管正向压降 [V]

$I_O$ : 输出电流 [A]

$t_{Dr}$ : 上升沿时 Deadtime [sec]

$t_{Df}$ : 下降沿时 Deadtime [sec]

$f_{SW}$ : 开关频率 [Hz]

Gate 电荷损耗

Gate 电荷损耗是 MOSFET Gate 充电引起的功率损耗。该损耗与高边及低边 MOSFET 的 Gate 电荷数(亦或 Gate 电容)有关，故 Gate 电荷损耗如下式算出。

$$P_G = (Q_{g-H} + Q_{g-L}) \times V_{gs} \times f_{sw} \quad [W] \quad (5)$$

或

$$P_G = (C_{g-H} + C_{g-L}) \times V_{gs}^2 \times f_{sw} \quad [W] \quad (6)$$

$Q_{g-H}$ : 高边 MOSFET 的 Gate 电荷数 [C]

$Q_{g-L}$ : 低边 MOSFET 的 Gate 电荷数 [C]

$C_{g-H}$ : 高边 MOSFET 的 Gate 电容 [F]

$C_{g-L}$ : 低边 MOSFET 的 Gate 电容 [F]

$V_{gs}$ : Gate 驱动电压 [V]

$f_{sw}$ : 开关频率 [Hz]

IC 的工作损耗

IC 的控制回路造成的功率损耗  $P_{IC}$  如下式算出。

$$P_{IC} = V_{IN} \times I_{CC} \quad [W] \quad (7)$$

$V_{IN}$ : 输入电压 [V]

$I_{CC}$ : IC 的工作电流 [A]

全功率损耗

IC 的功率损耗 P，将上述损耗全部相加。

$$P = P_{ON-H} + P_{ON-L} + P_{SW-H} + P_D + P_G + P_{IC} \quad [W] \quad (8)$$

$P_{ON-H}$ : 导通损耗(高边) [W]

$P_{ON-L}$ : 导通损耗(低边) [W]

$P_{SW-H}$ : Switching 损耗(高边) [W]

$P_D$ : Deadtime 损耗 [W]

$P_G$ : Gate 电荷损耗 [W]

$P_{IC}$ : IC 的工作损耗 [W]

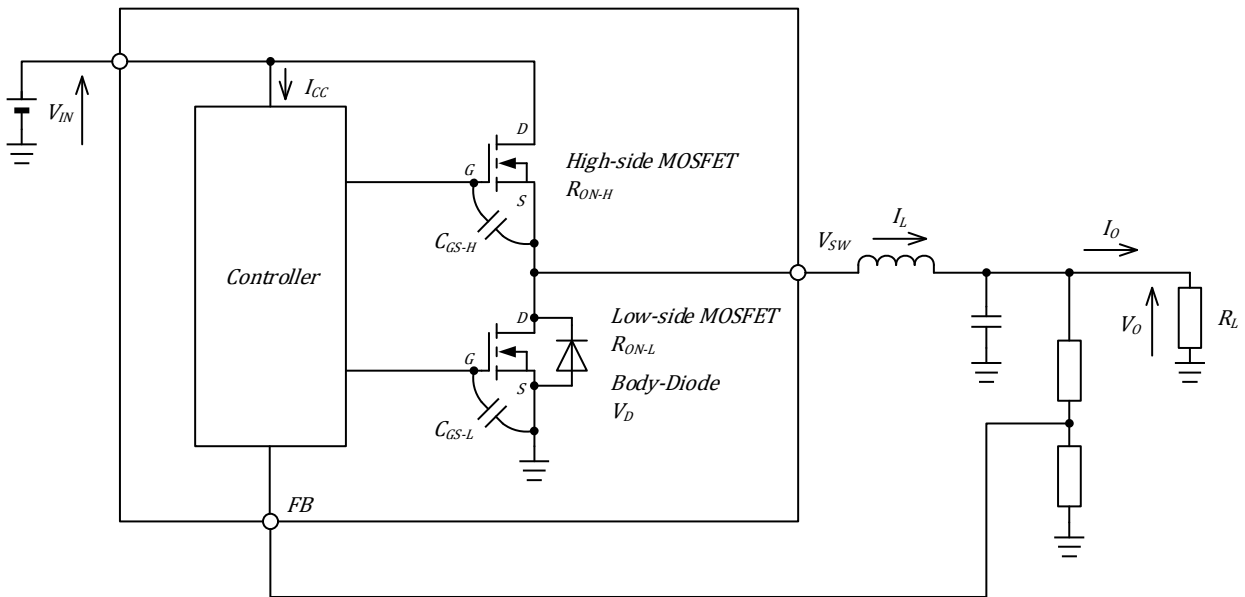


Figure 1. 同步整流型 DC/DC 变换器回路图

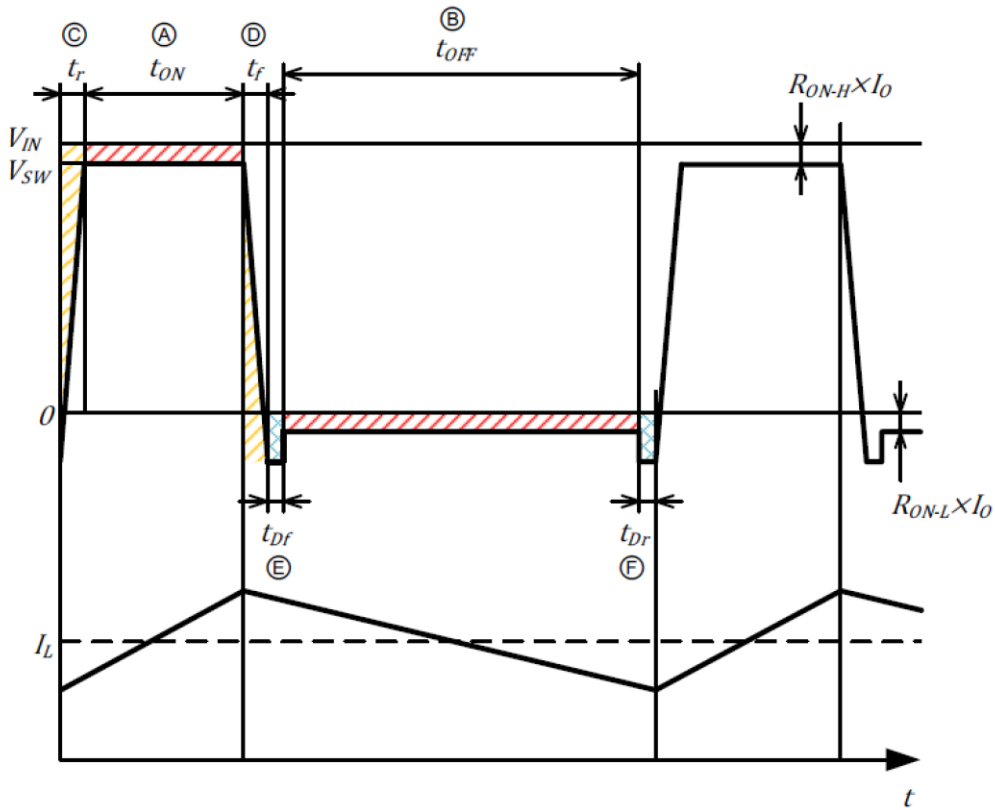


Figure 2. Switching 波形与损耗

计算例

计算式	Parameter	结果
1. 导通损耗 $P_{ON-H} = I_O^2 \times R_{ON-H} \times \frac{V_O}{V_{IN}}$ $P_{ON-L} = I_O^2 \times R_{ON-L} \times \left(1 - \frac{V_O}{V_{IN}}\right)$	$V_{IN}$ : 输入电压 12 V $V_O$ : 输出电压 5.0 V $I_O$ : 输出电流 3.0 A $R_{ON-H}$ : 高边 MOSFET ON 电阻 100 mΩ $R_{ON-L}$ : 低边 MOSFET ON 电阻 70 mΩ	375 mW 367.5 mW
2. Switching 损耗 $P_{SW-H} = \frac{1}{2} \times V_{IN} \times I_O \times (t_r + t_f) \times f_{SW}$	$f_{SW}$ : 开关频率 2.0 MHz $t_r$ : 高边 MOSFET 上升沿时间 4 nsec $t_f$ : 高边 MOSFET 下降沿时间 6 nsec	360 mW
3. Deadtime 损耗 $P_D = V_D \times I_O \times (t_{Dr} + t_{Df}) \times f_{SW} \quad [W]$	$V_D$ : 低边 MOSFET 体二极管正向压降 0.5 V $t_{Dr}$ : 上升沿时 Deadtime 30 nsec $t_{Df}$ : 下降沿时 Deadtime 30 nsec	180 mW
4. Gate 电荷损耗 $P_G = (Q_{g-H} + Q_{g-L}) \times V_{gs} \times f_{SW}$ $P_G = (C_{g-H} + C_{g-L}) \times V_{gs}^2 \times f_{SW}$	$Q_{g-H}$ : 高边 MOSFET 的 Gate 电荷数 1 nC $Q_{g-L}$ : 低边 MOSFET 的 Gate 电荷数 1 nC $C_{g-H}$ : 高边 MOSFET 的 Gate 电容 200 pF $C_{g-L}$ : 低边 MOSFET 的 Gate 电容 200 pF $V_{gs}$ : Gate 驱动电压 5.0V	20 mW
5. IC 的工作损耗 $P_{IC} = V_{IN} \times I_{CC}$	$I_{CC}$ : IC 的消费电流 1.0 mA	12 mW
全功率损耗 $P = P_{ON-H} + P_{ON-L} + P_{SW-H} + P_D + P_G + P_{IC}$		1.31 W

MOSFET 的 Gate 电容及体二极管正向压降等，IC 的内部参数一般厂商未必公开。该情况下，使用计算例里的值，可以进行大致的估算。

## Notes

- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.  
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products specified in this document are not designed to be radiation tolerant.
- 7) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 8) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 9) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 10) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 11) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 12) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 13) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.  
More detail product informations and catalogs are available, please contact us.

## ROHM Customer Support System

<http://www.rohm.com/contact/>