

TI-RSLK

Texas Instruments Robotics System Learning Kit



TEXAS INSTRUMENTS

Module 12


Lecture: DC motors - Physics



DC motors

You will learn in this module

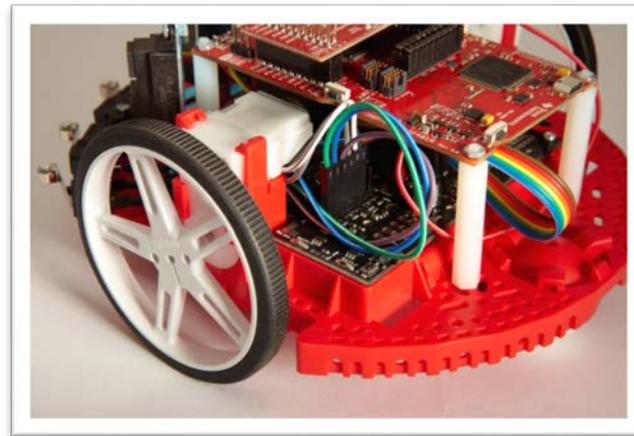- Fundamentals of Electromagnetic Fields
 - Ampere's Law
 - Faraday-Maxwell
- Brushed DC Motors







Electromagnetic Fields

Current induces a magnetic field

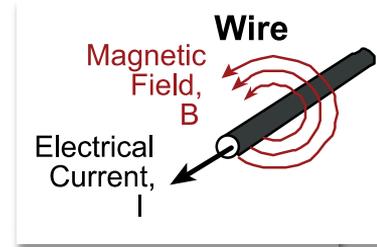- Derived from Ampere's Law: $B = NI\mu/L$
- I is current
- L is the length of the coil
- N is the number of turns
- μ is the permeability
- B is magnetic field



Electromagnet

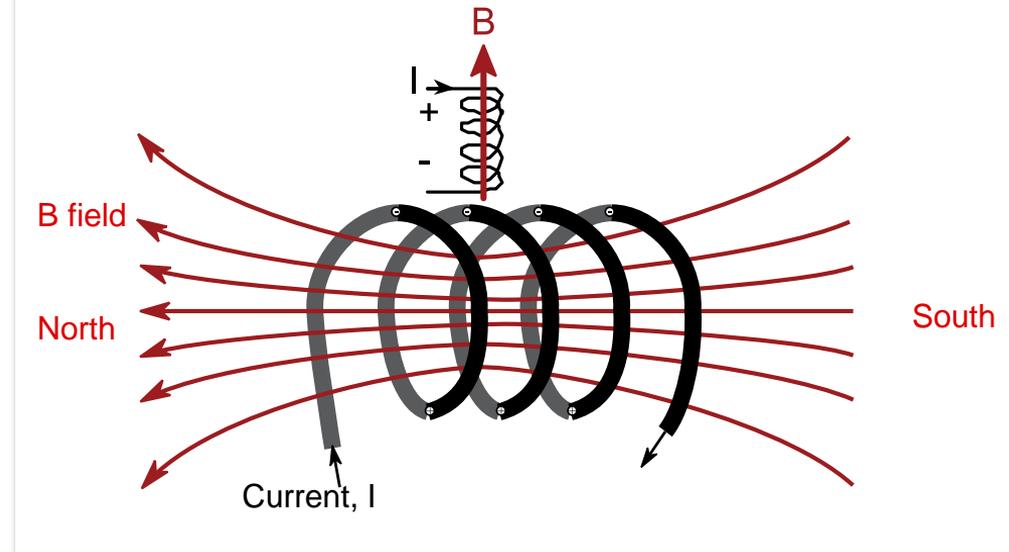



DC Motor Physics

Faraday-Maxwell

Force = Current*Length*Magnetic Field


$$F = I * L * B$$

Right hand rule



Thumb = direction of current

Fingers = direction of magnetic field

Palm = direction of force

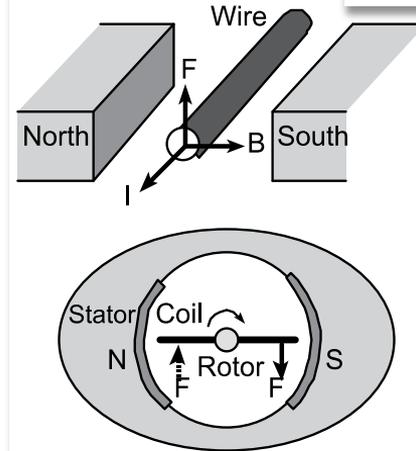

Electrical Model

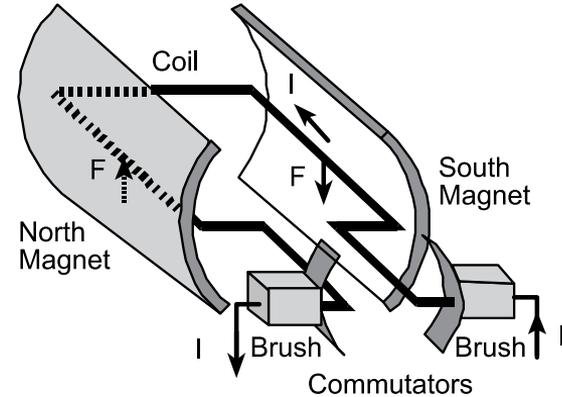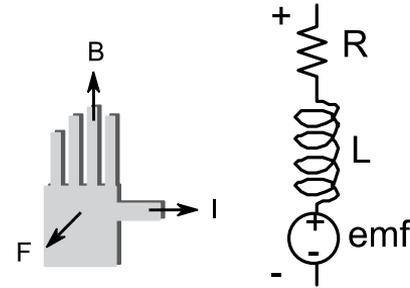





DC Motor Physics

Electrical Model

R - Resistance from long wires

L - Inductance because wires are coil (electromagnet)

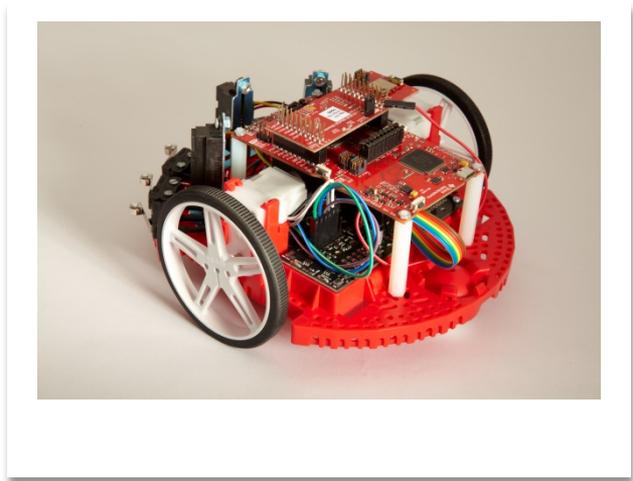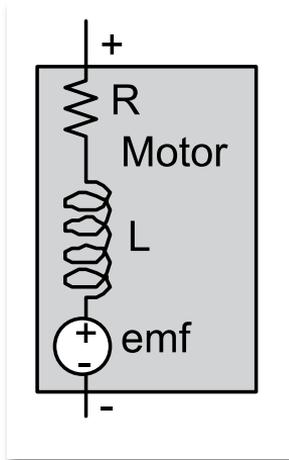emf - voltage (mechanical ↔ electrical energy conversion)




$$V = L \frac{di}{dt}$$



DC Motor Physics

Components

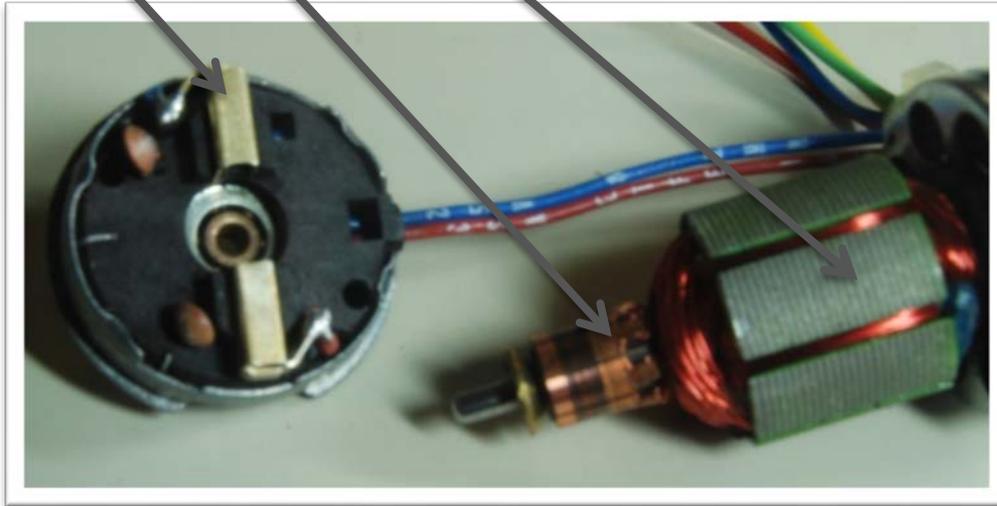Brushes Commutator Rotor Stator (not shown)






Basic Model for a DC motor

Considerations

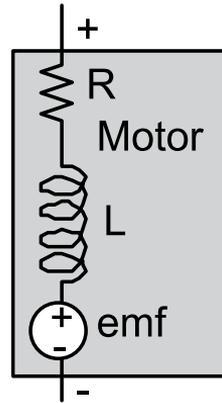- Voltage (V)
- Current (A)
- Power ($W = V \cdot A = J/sec$)
- Force ($N = kg \cdot m/sec^2$)
- Torque ($N \cdot m$)
- Inductance (H)
- emf (V)
- Friction (coefficient)
- Speed (rps)




$$P = V \cdot I$$

$$F = m \cdot a$$

$$\tau = F \cdot d$$

$$V = L \, dl/dt$$

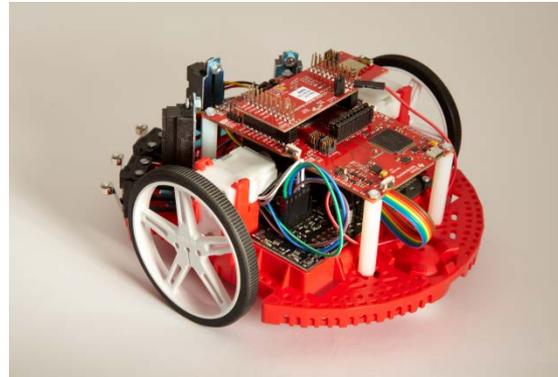





Summary

Electromagnets

- $B = NI\mu/L$

DC Motor

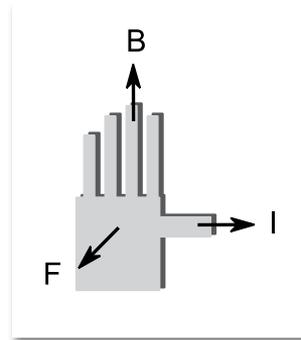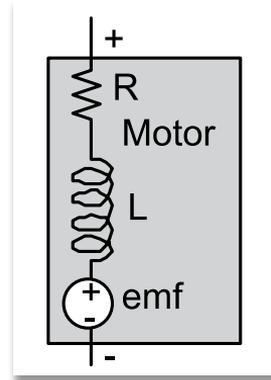- $F = I * L * B$
- R, L, emf
- Brush, commutator, coil, stator
- Power, force, torque



Right hand rule

Thumb = direction of current

Fingers = direction of magnetic field

Palm = direction of force

Module 12


Lecture: DC motors - Interface



DC motors

You will learn in this module

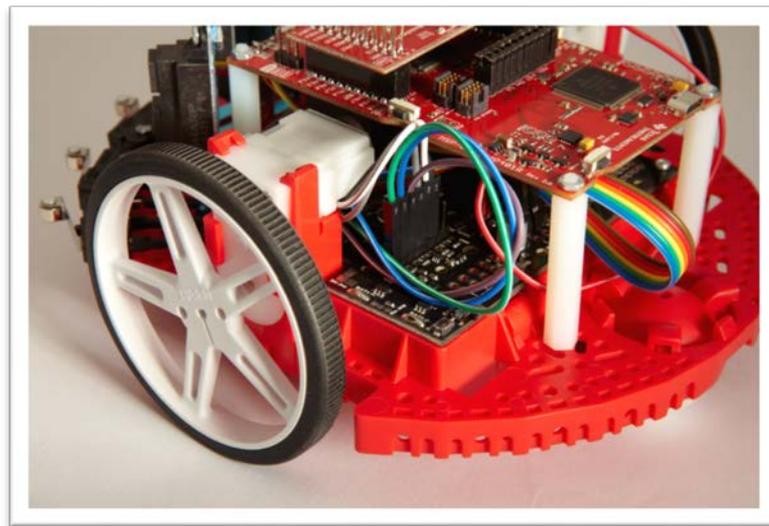- Drive circuits for DC Motors
 - Darlington Pair, H bridge
 - TI DRV8838 driver
 - Interfacing motors with TI's LaunchPad





Basic Drive circuits for DC motors

Design considerations

- Peak voltage
- Peak current
- Speed
- Back emf

$$V = V_m - V_{ce}$$


$$I_b = I_{ce}/h_{fe} \text{ (max)}$$

$$R < (3.3 \cdot V_{be})/I_b$$

$$R = 30\Omega$$

Why is $I > (V_m - V_{ce})/30\Omega$?

$$emf = (V_m - V_{ce}) - I_m \cdot R$$

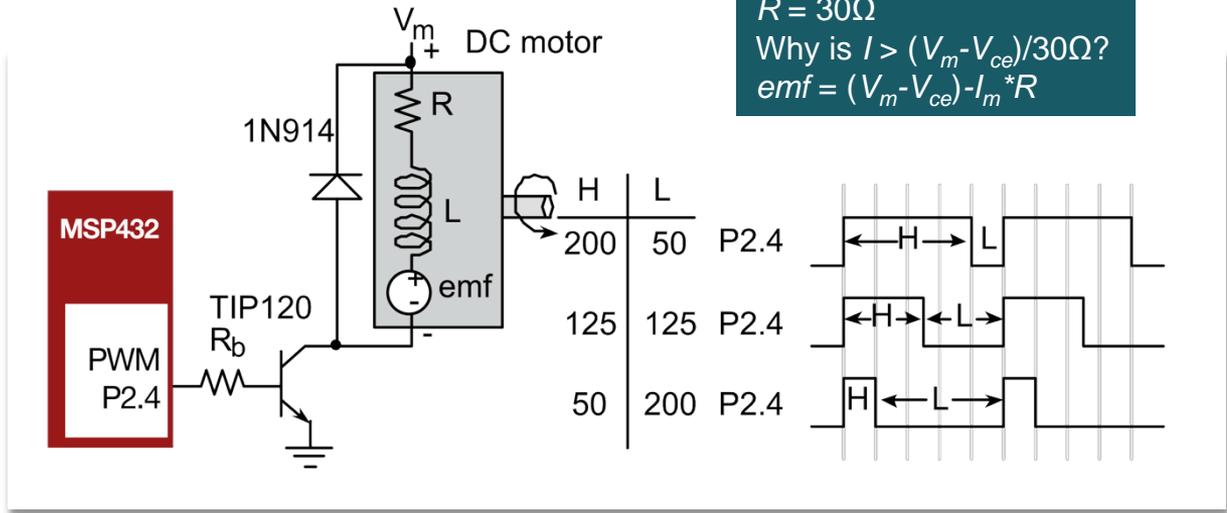

One direction, power adjusted by duty cycle



Basic Drive circuit – Unidirectional

Design: 6V, 1A

- TIP120 (NPN)
- $h_{fe} = 1000$ (typical)
- $I_{ce} = 3A$ (max)
- back emf (1N914)


$$I_b = I_{coil} / h_{fe} = 1A / 1000 = 1mA$$

$$R_b \leq (V_{OH} - V_{be}) / I_b = (3 - 2.5) / 1mA = 0.5 \text{ k}\Omega$$

$$R_b = 100 \Omega$$

V_{CE} depends on current (0.5 to 1 V)

$$V = L \frac{dI}{dt}$$

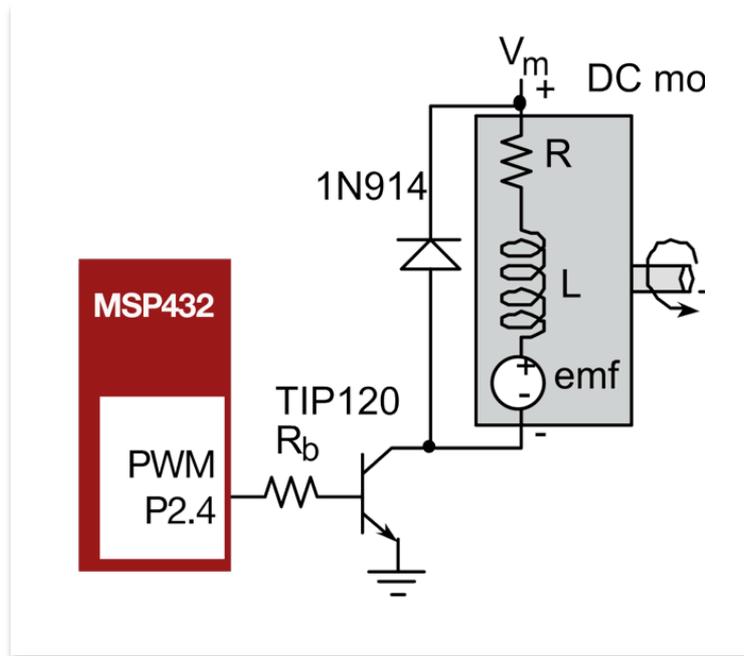




MOSFET Drive circuit for DC motor

N channel considerations

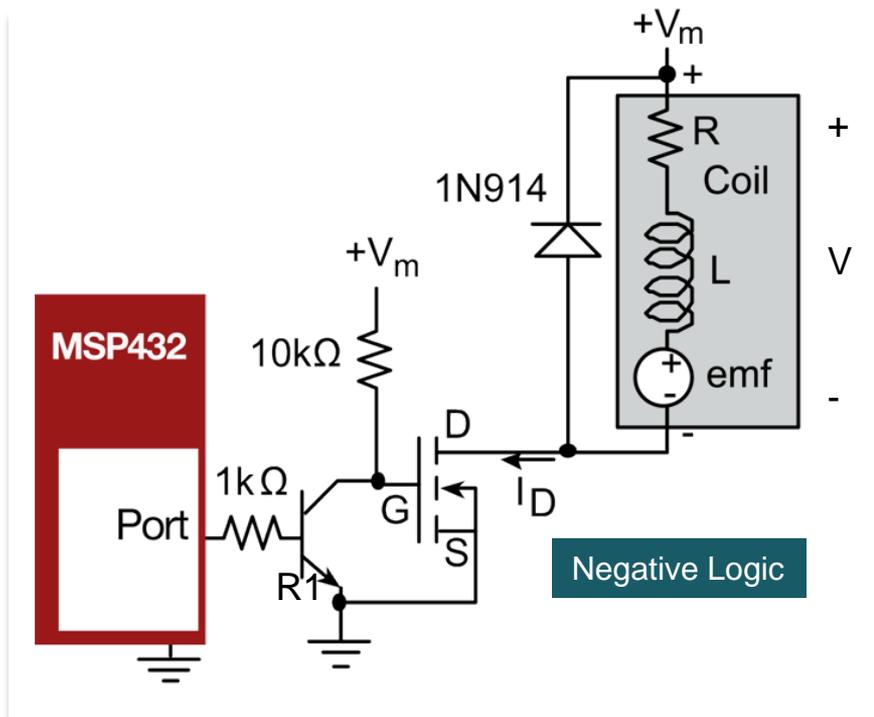- V_{GS} turns on
- V_{DS} small
- I_{DS} large



$$V = V_m - V_{DS}$$

$$I_b = I_{ce}/h_{fe} (\text{max})$$


$$R1 < (3.3 - V_{be})/I_b$$



Motor-Drive Circuits for Bidirectional Control

H bridge using Two-phase Motor Driver (TI L293)

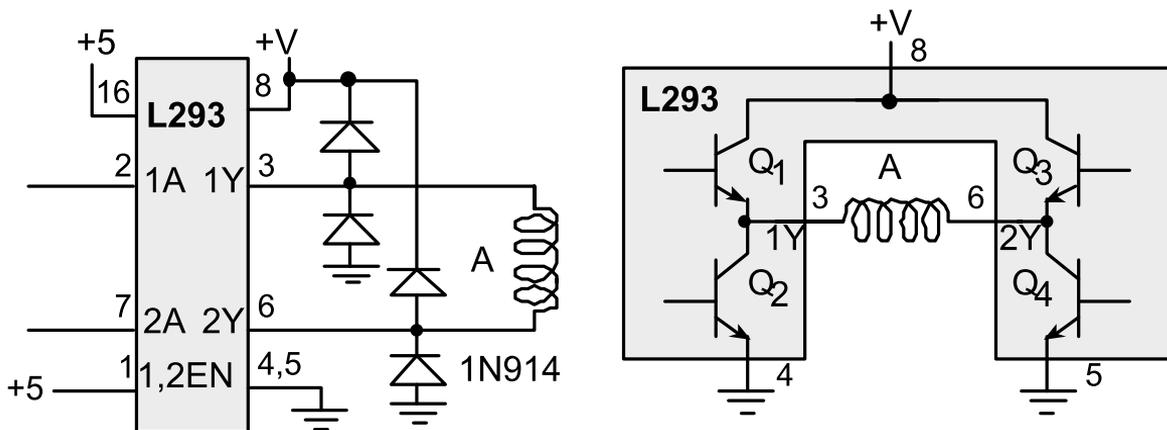- Can spin motors in both directions
- Can lose 1 to 2 V in transistors




More information: <http://www.ti.com/lit/ds/symlink/l293.pdf>



MOSFET interface of a DC motor

P channel considerations

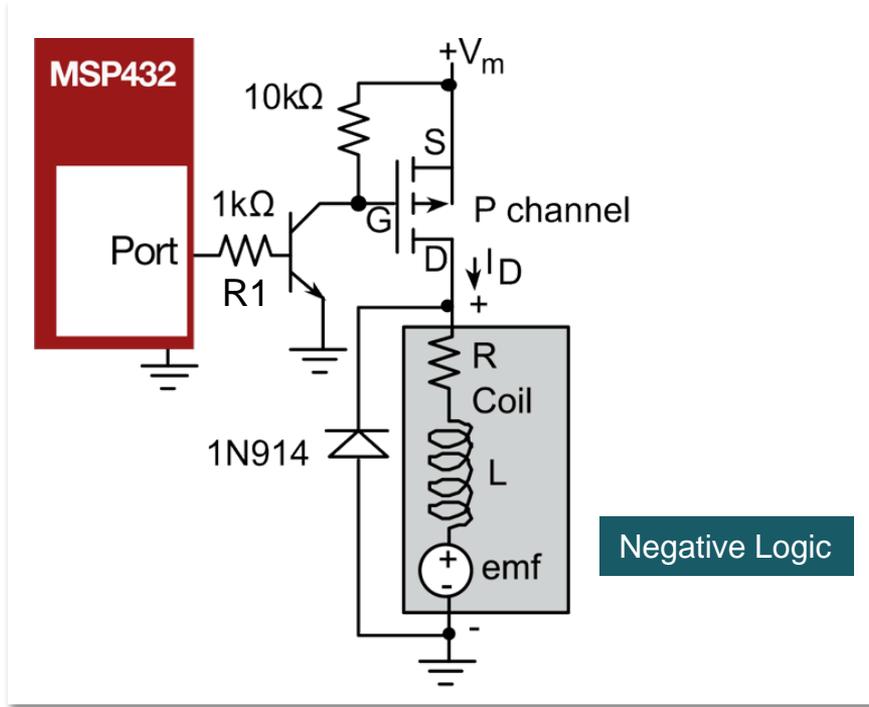- V_{GS} turns on
- V_{DS} small
- I_{DS} large



$$V = V_m - V_{DS}$$


$$I_b = I_{ce}/h_{fe} (\text{max})$$

$$R1 < (3.3 - V_{be})/I_b$$



MOSFET interface of a DC motor using H bridge

H bridge

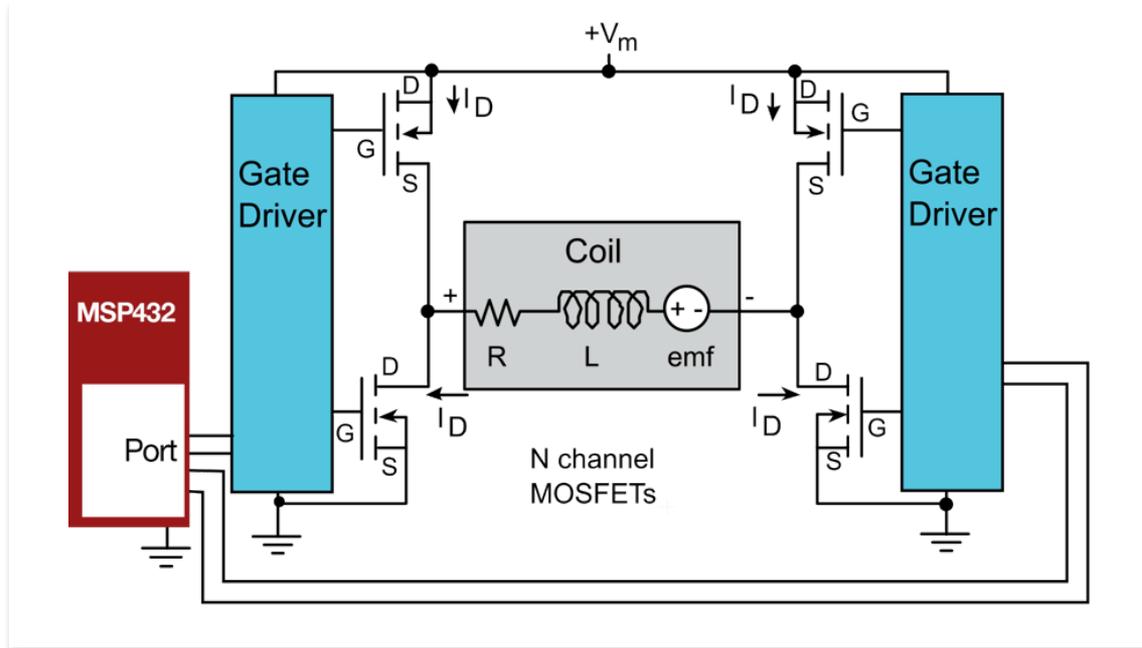

Basic circuit inside the DRV8838


More info: <http://www.ti.com/product/drv8838/description?keyMatch=DRV8838&tisearch=Search-EN-Everything>



Drive circuit using TI DRV8838

$R_{DS} = 0.28\Omega$

Pololu Board

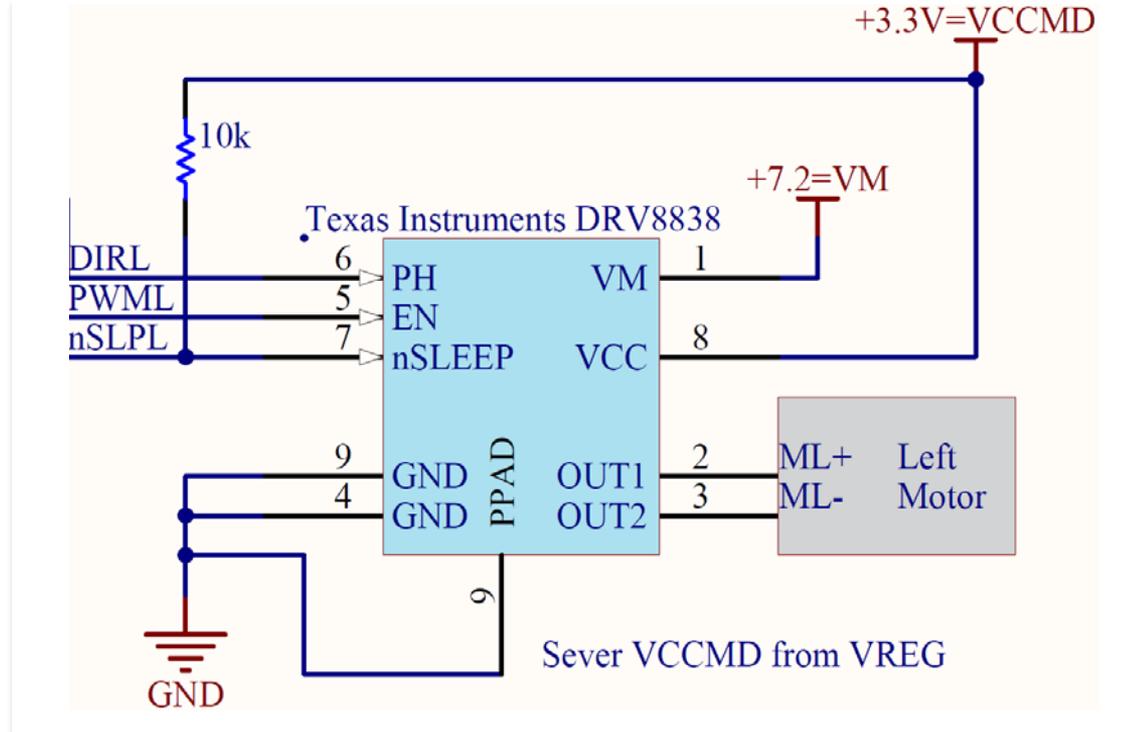


More info: <http://www.ti.com/product/drv8838/description?keyMatch=DRV8838&tisearch=Search-EN-Everything>

Drive circuit waveforms for DC Motors

DRV8838


Times < 200ns

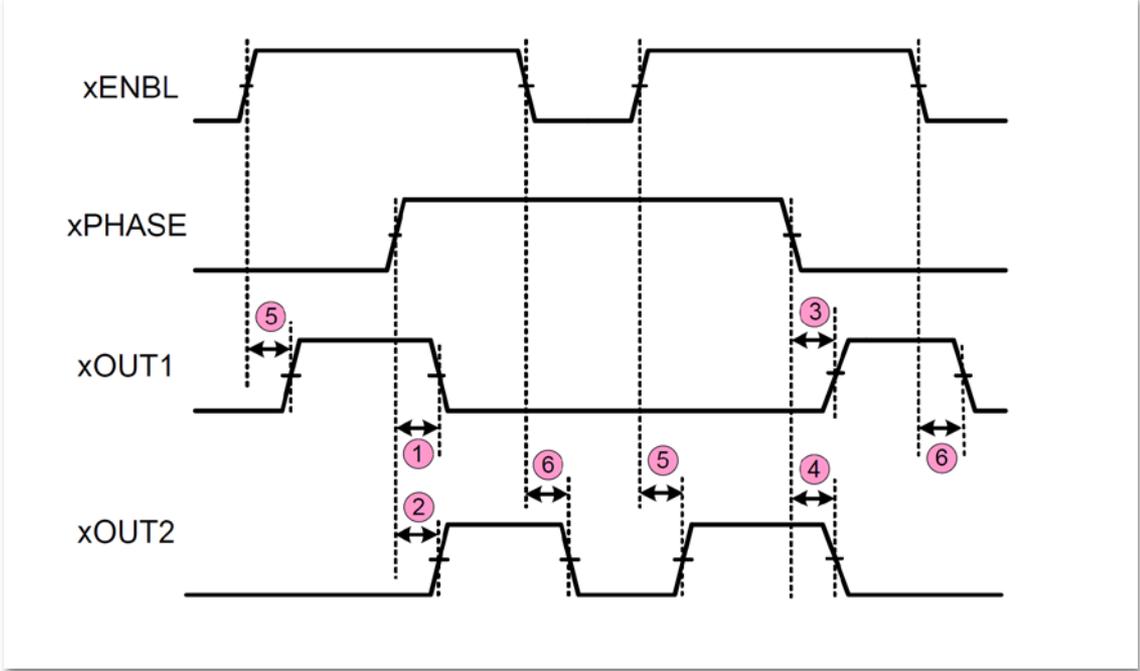

More info: <http://www.ti.com/product/drv8838/description?keyMatch=DRV8838&tisearch=Search-EN-Everything>



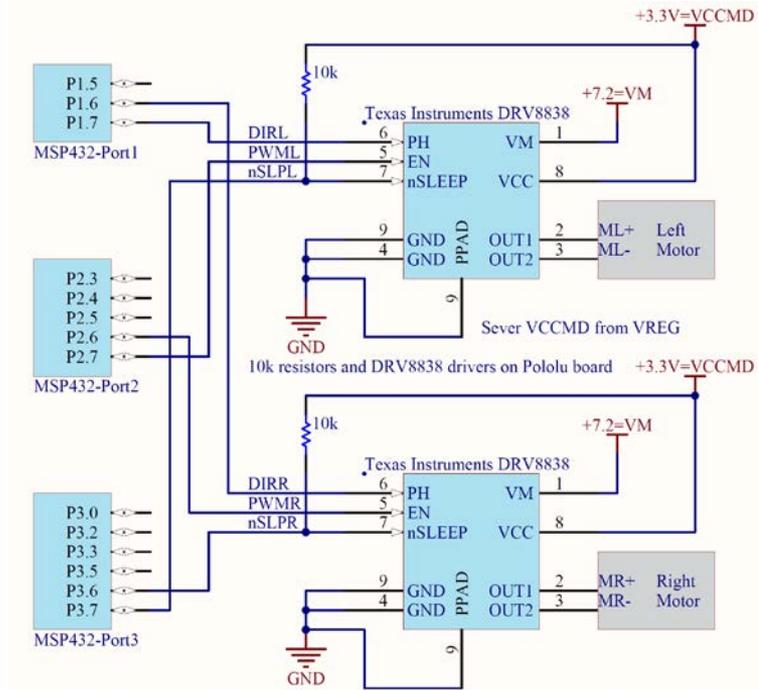Motor Drive and Power distribution board interface with TI's Launchpad Development board




P3.6=P3.7=1 to activate, not sleep

PH	EN	
DIRL	PWML	
P1.7	P2.7 Left	
0	0	Stop
1	0	Stop
0	1	Forward
1	1	Back

PH	EN	
DIRR	PWMR	
P1.6	P2.6 Right	
0	0	Stop
1	0	Stop
0	1	Forward
1	1	Back

Pololu Board

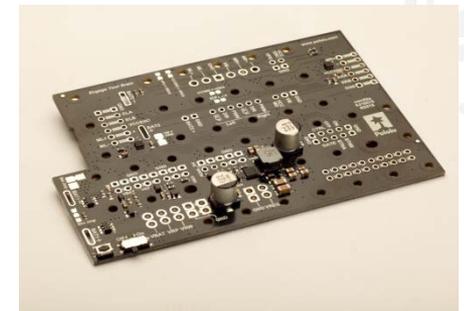



Summary

Darlington interfaces



- Simple, inefficient

MOSFET interfaces

- Efficient, large current

H bridge Interfaces

- Both directions
- DRV8838

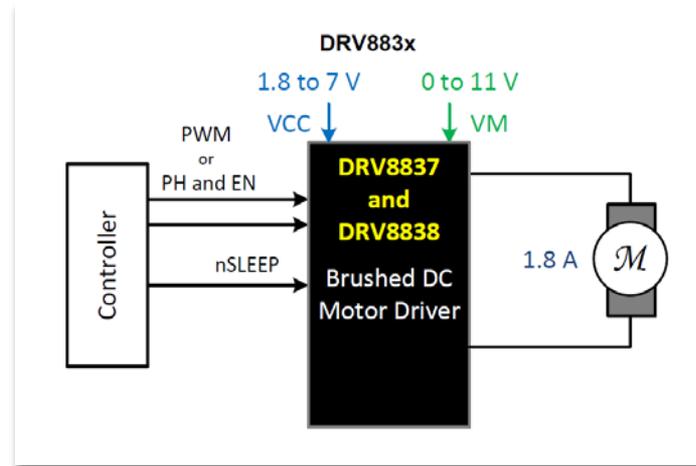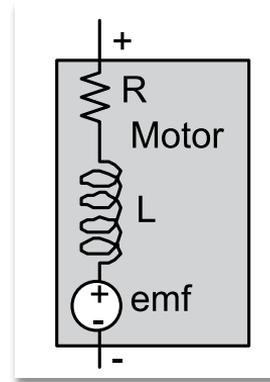

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated