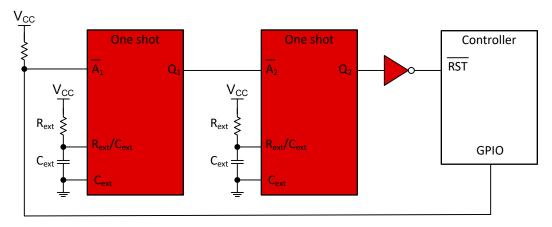
Detect and Reset an Unresponsive Controller



System controllers that are critical to system operation can use a monostable multivibrator pair to detect if the system has become unresponsive and reset the system. By sending a pulse every few miliseconds to a multivibrator pair, a reset pulse is sent if the signal stays at a constant high or low.



Example System Diagram With Pull-up Resistor and Falling-edge Trigger

Design Considerations

- The first monostable multivibrator must be retriggerable
- The output pulse length of the multivibrator must be longer than the period of the keep-alive signal. The
 pulse length of a multivibrator is T=kRC. The recommended configuration is a 100-kΩ resistor and a 0.1-uF
 capacitor, for a pulse length of around 10 ms.
- Either falling-edge or rising-edge trigger configurations can be used for this application. See the datasheet of your selected multivibrator for details.
- A pull-up or pull-down resistor is required to hold the input at a valid state during reset. The recommended value for this resistor is $10 \text{ k}\Omega$.
- [FAQ] [H] Monostable Multivibrators Top Questions Answered
- [FAQ] How does a slow or floating input affect a CMOS device?
- Ask a question on our E2E[™] forum

Recommended Parts

Part Number	Automotive Qualified	V _{CC} Range	Function	Features
SN74LVC1G123		1.65 V–5.5 V	Single channel multivibrator	Retriggerable, Schmitt-trigger inputs
SN74LV123A	✓	2 V–5.5 V	Dual channel multivibrator	Retriggerable, Inverted output, Schmitt-trigger inputs
SN74LV123A-Q1				
CD74HC4538		2 V–6 V	Dual channel multivibrator	Retriggerable, Inverted output
CD74HC4538-Q1	✓			
SN74AHC1G04		2 V — 5.5 V	Single channel inverting buffer	
SN74AHC1G04-Q1	✓			

For more devices, browse through the *online parametric tool* where you can sort by desired voltage, channel numbers, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2023, Texas Instruments Incorporated